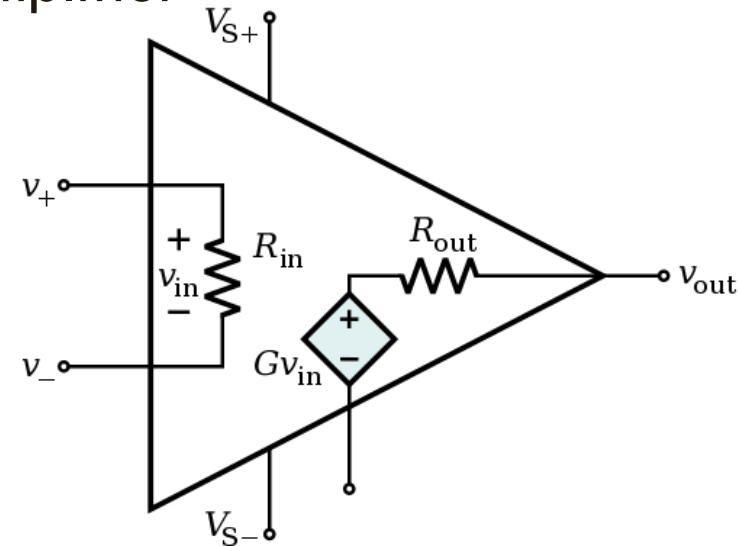




# BIOPOTENTIAL AMPLIFIERS


# Op Amp Basics

- Op Amp is a high-gain differential amplifier
- Ideal Op Amp characteristics:
  - ▣ Gain is infinite
  - ▣ Input impedance is infinite
  - ▣ Output impedance is infinite
  - ▣ Bandwidth is infinite
- Ideal Op Amp rules for circuit design:
  - ▣  $V^+ = V^-$  (input terminals have same voltage)
  - ▣  $i^+ = i^-$  (no current through input terminals)
- Basic design approach: design Op Amp circuit using ideal rules then check practical issues



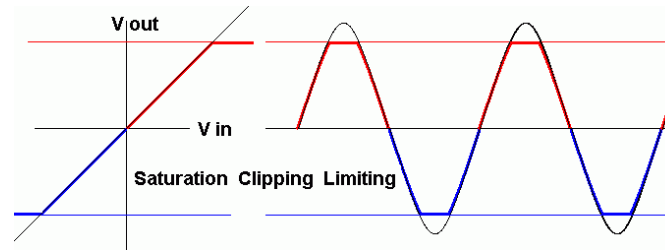
# Practical Issues

- Linear range limitations (saturation)
  - ▣ Depends on power supply range (slightly less) and Op Amp type



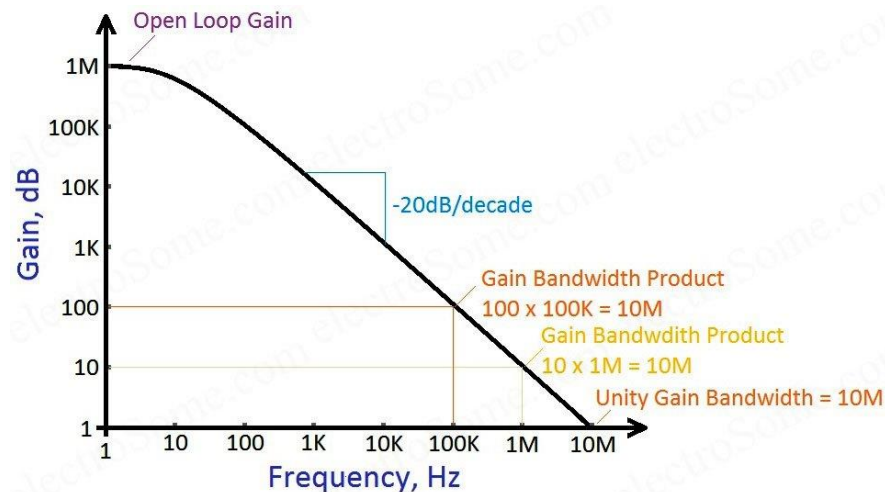
- Gain-Bandwidth Product = Constant for a given Op Amp
  - ▣ Maximum gain determined by bandwidth of signal for a given Op Amp


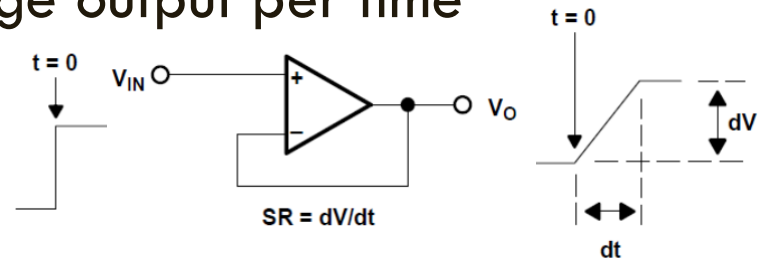
# Practical Issues


- Slew Rate: rate of change of voltage output per time

- ▣ Identify maximum input frequency and amplitude applicable to amplifier such that output is not significantly distorted




- Offset voltage: small voltage between  $V^+$  and  $V^-$

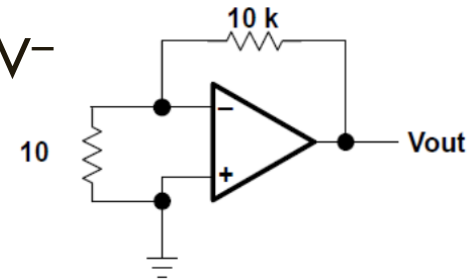- ▣ Offset nulling available in some Op Amps
- ▣ May also drift with time



- Bias Current: small currents flowing into  $i^+$  and  $i^-$

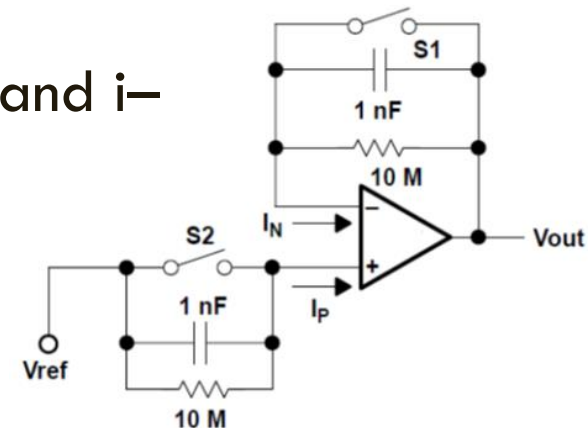- ▣ Always use DC coupling for input terminals




# Practical Example: 741 Op Amp


Bandwidth (Note 6)	1.5	MHz
Slew Rate	0.7	V/ $\mu$ s

Output Voltage Swing	$V_S = \pm 20V$
----------------------	-----------------


Parameter	Test Conditions	LM741A			LM741			LM741C			Units
		Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	
Input Offset Voltage	$T_A = 25^\circ\text{C}$ $R_S \leq 10\text{ k}\Omega$ $R_S \leq 50\Omega$		0.8	3.0		1.0	5.0		2.0	6.0	mV
	$T_{AMIN} \leq T_A \leq T_{AMAX}$ $R_S \leq 50\Omega$ $R_S \leq 10\text{ k}\Omega$			4.0			6.0			7.5	mV
Input Offset Current	$T_A = 25^\circ\text{C}$		3.0	30		20	200		20	200	nA
	$T_{AMIN} \leq T_A \leq T_{AMAX}$			70		85	500			300	

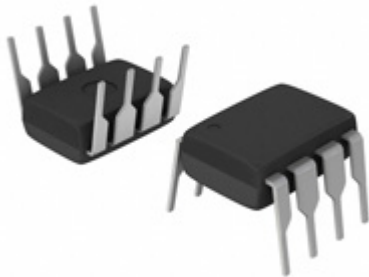





Dual-In-Line or S.O. Package

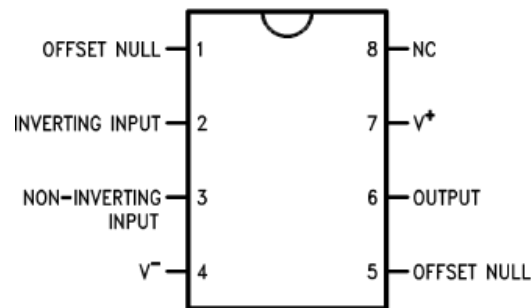




Offset Nulling Circuit

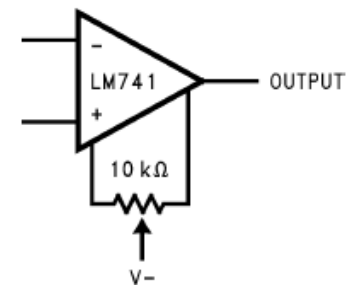


# Example Basic Op Amp Circuits

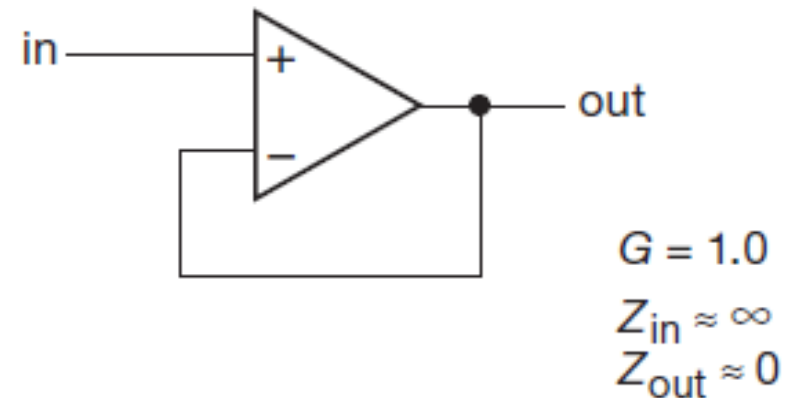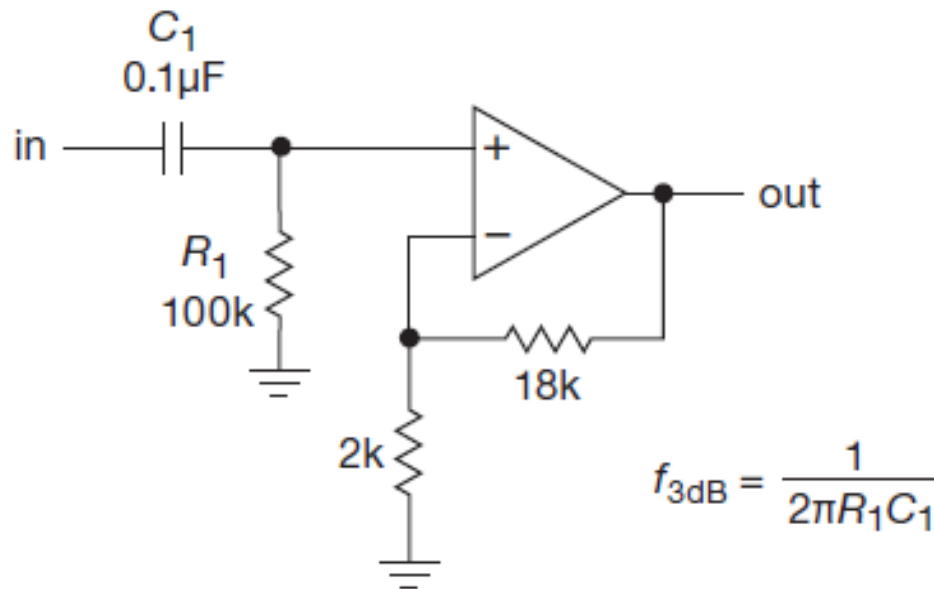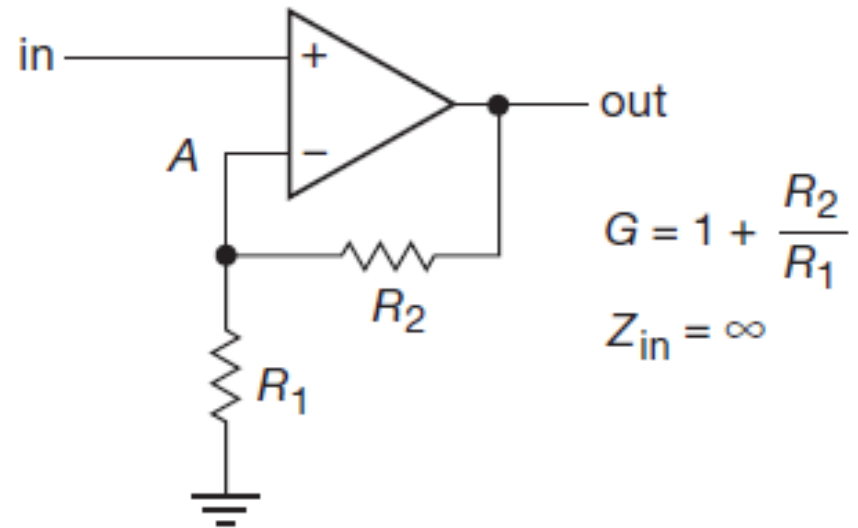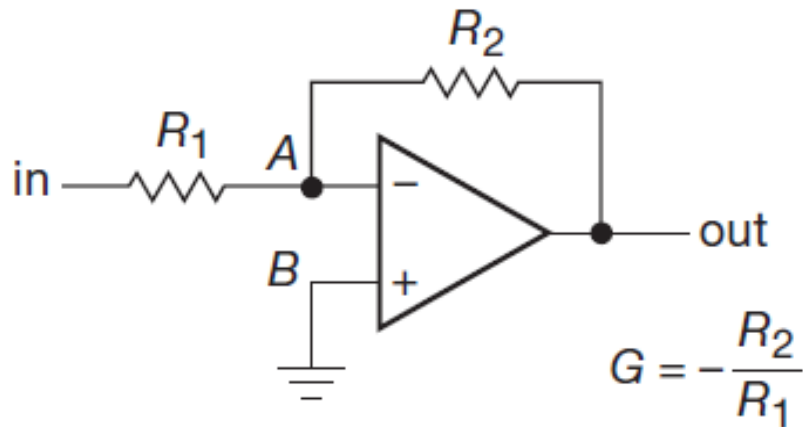



# Example Basic Op Amp Circuits

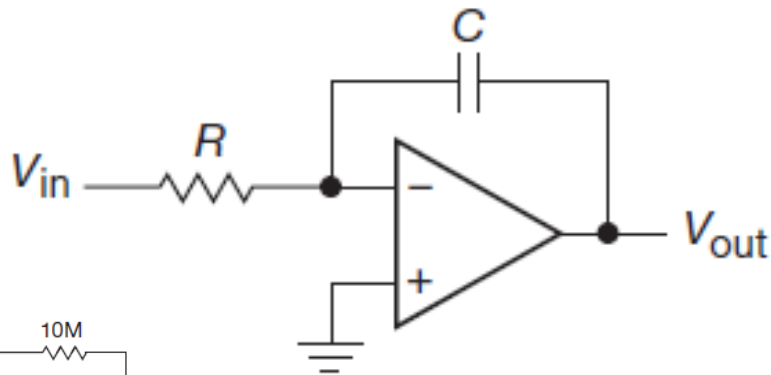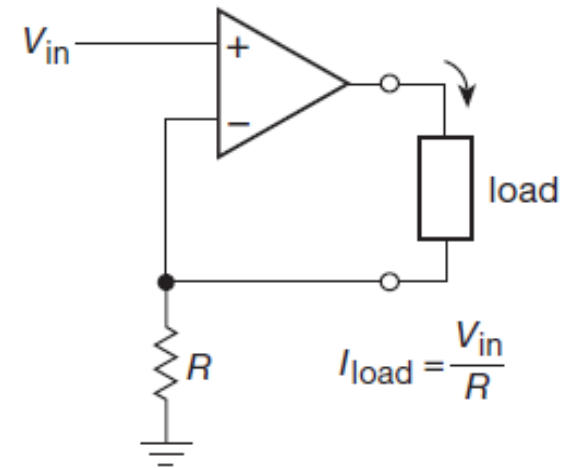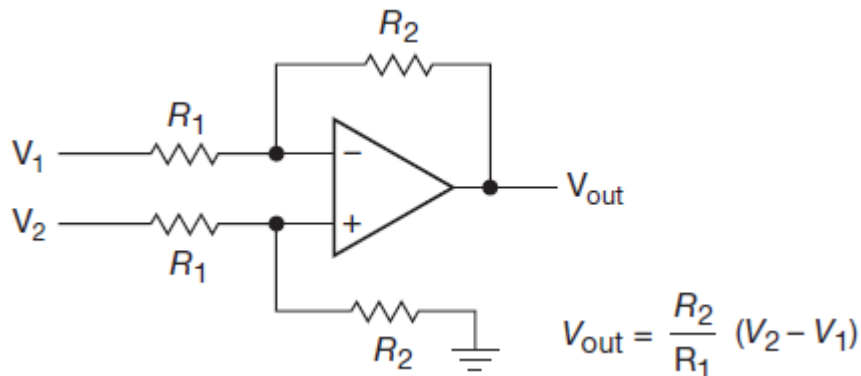


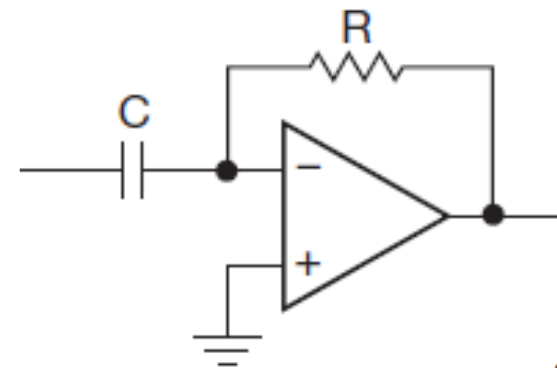
$$V_{out}(t) = -\frac{1}{RC} \int V_{in}(t) dt + \text{const.}$$



$$V_{out} = -RC \frac{dV_{in}}{dt}$$

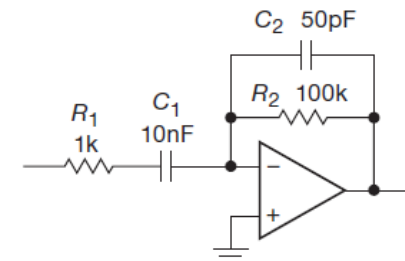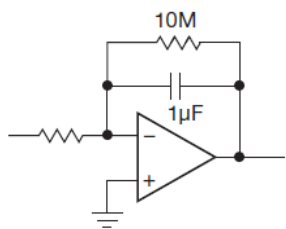



# Photodiode/Transistor Amplifier

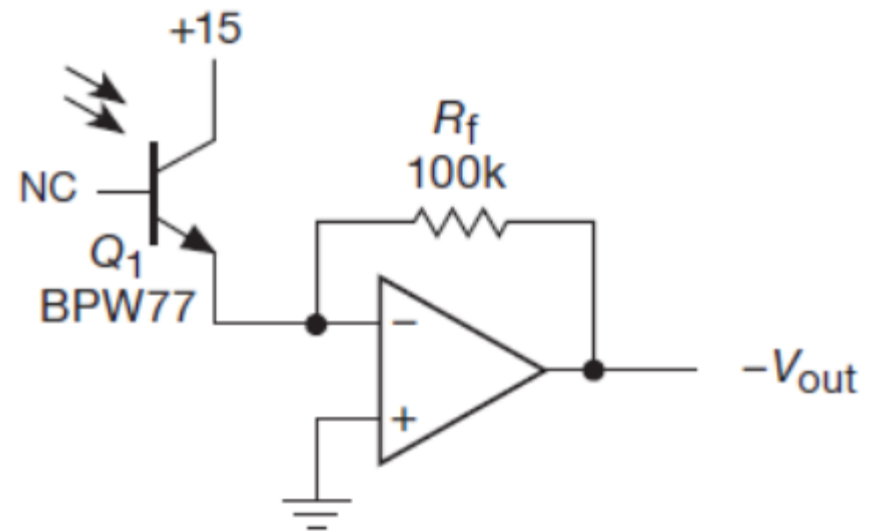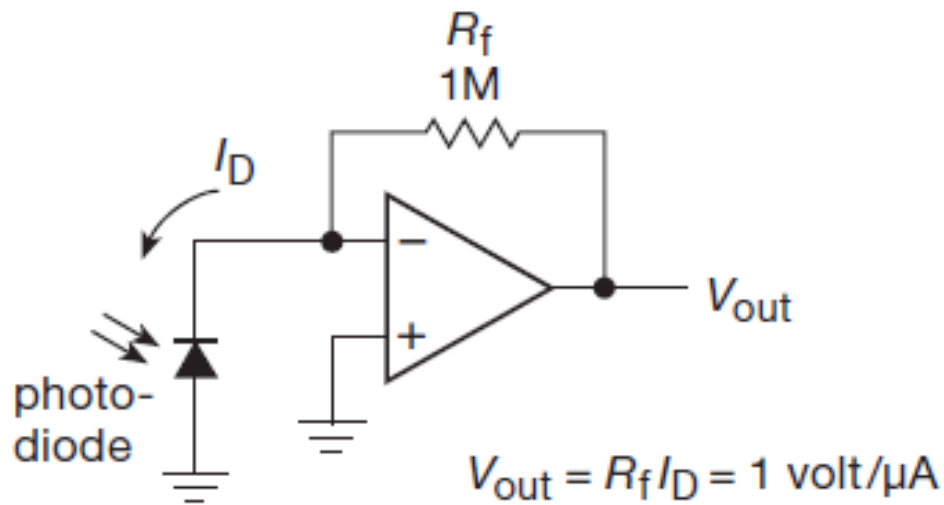





# Comparator



## Op Amp without Feedback

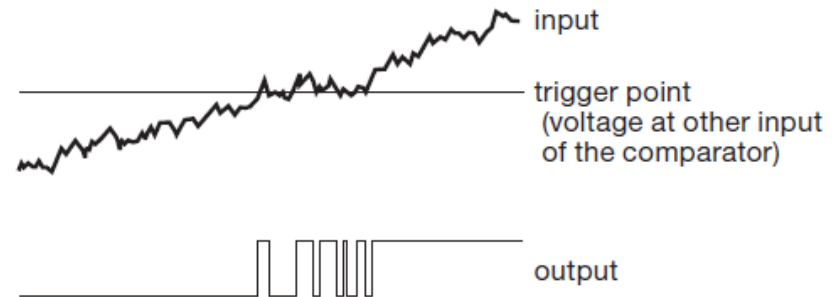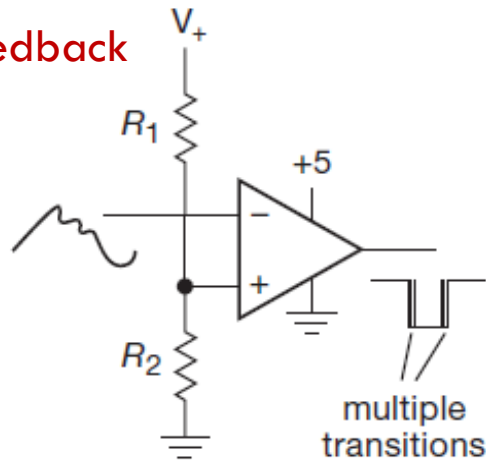

## Schmitt Trigger

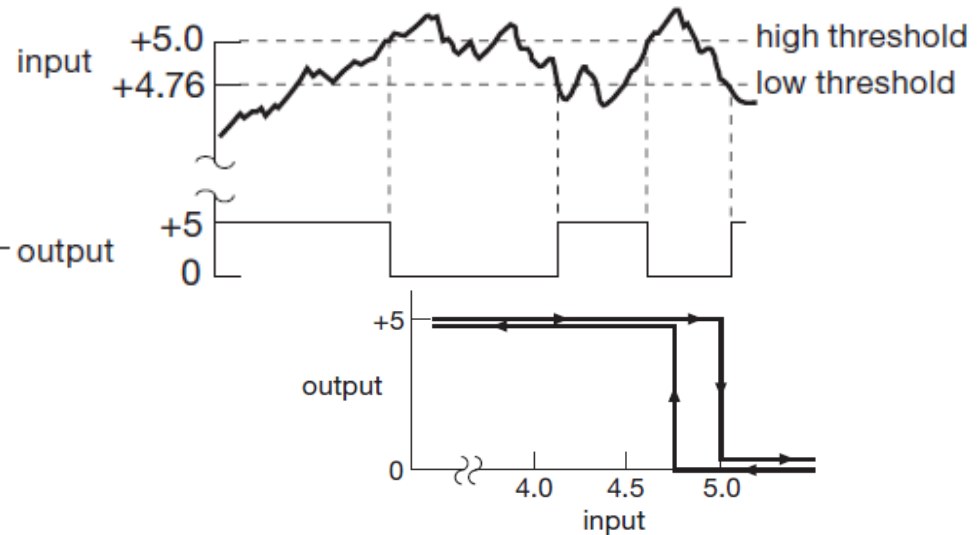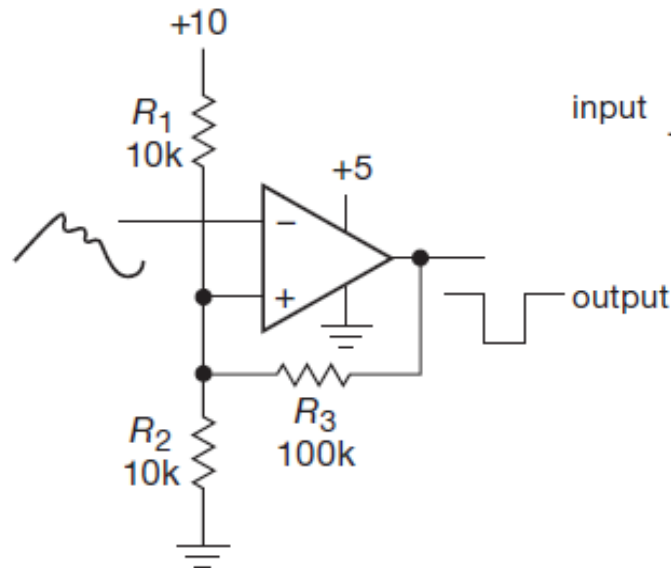


# Power Switching

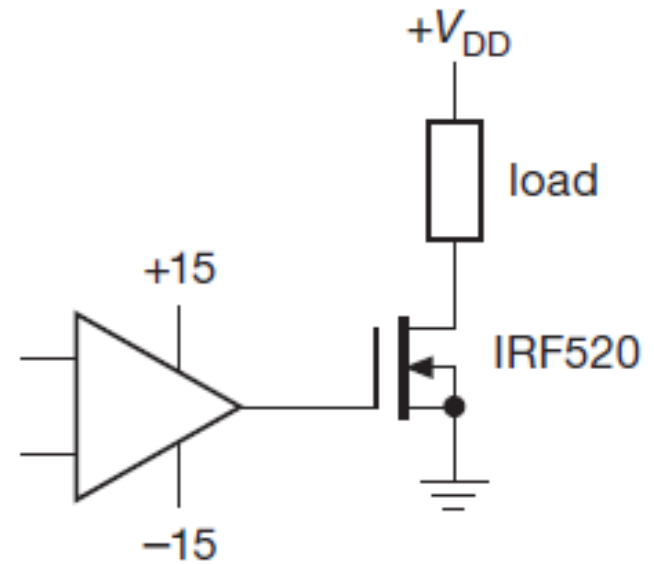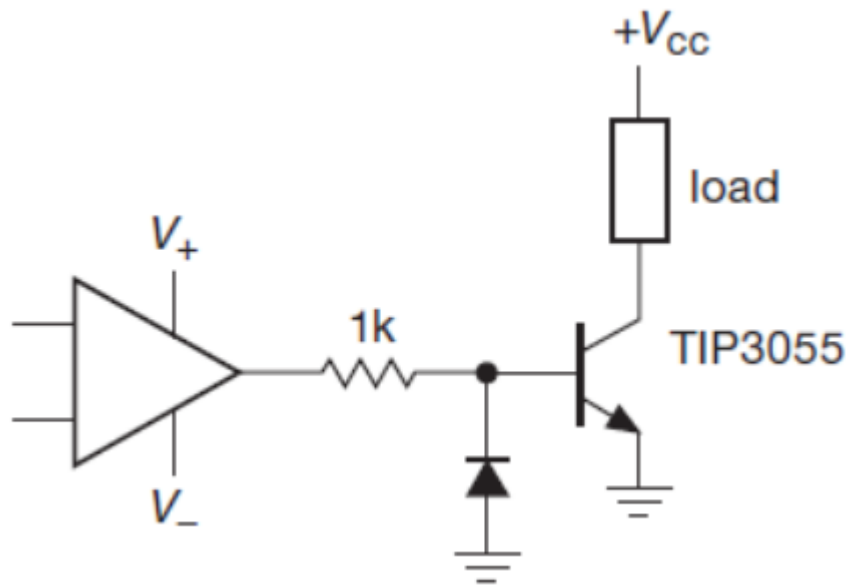


Note: Diode snubber is needed if load is inductive

# Active Half-Wave Rectifier

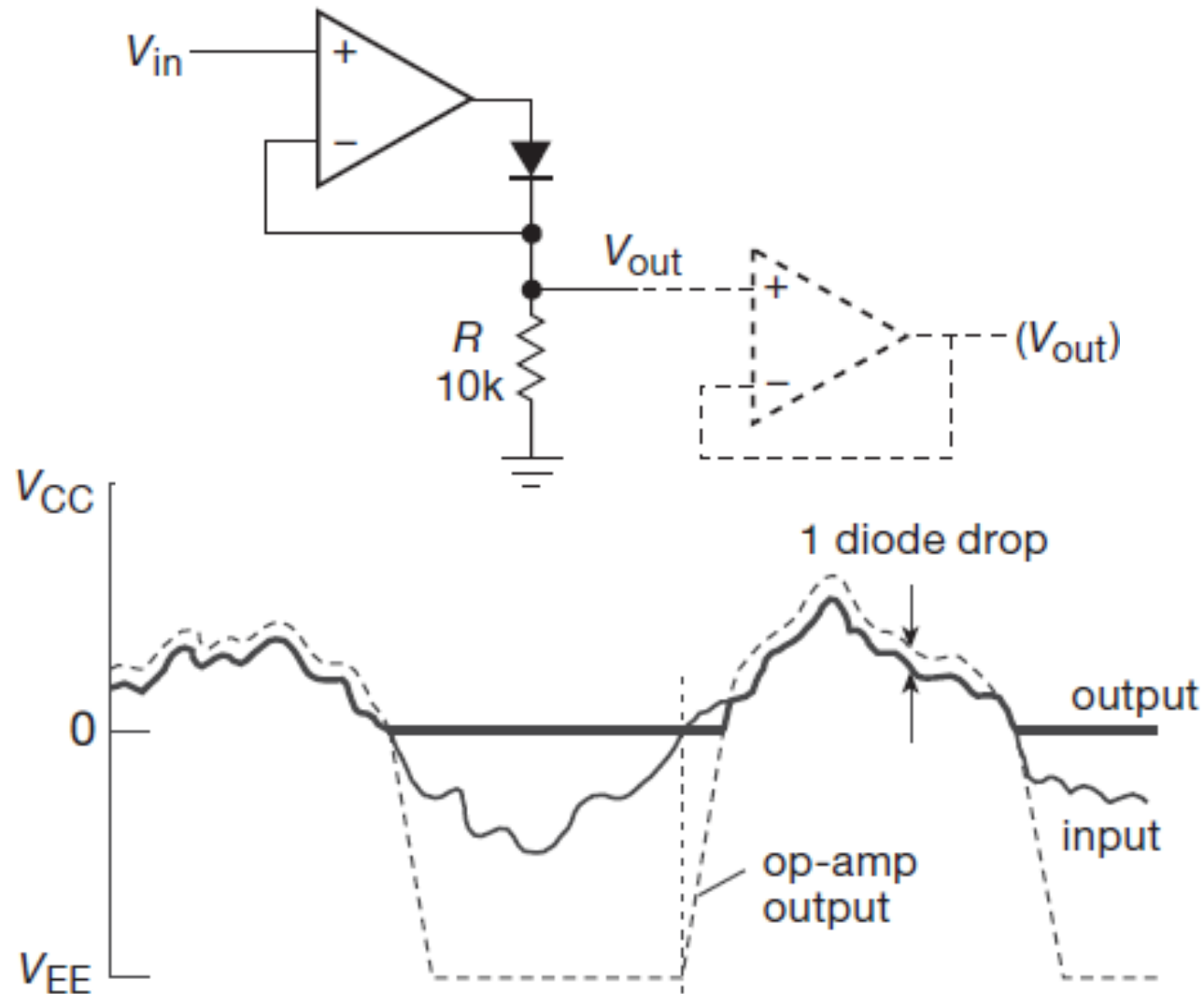

# Absolute-Value and Log Amplifiers



## □ Active full-wave rectifier

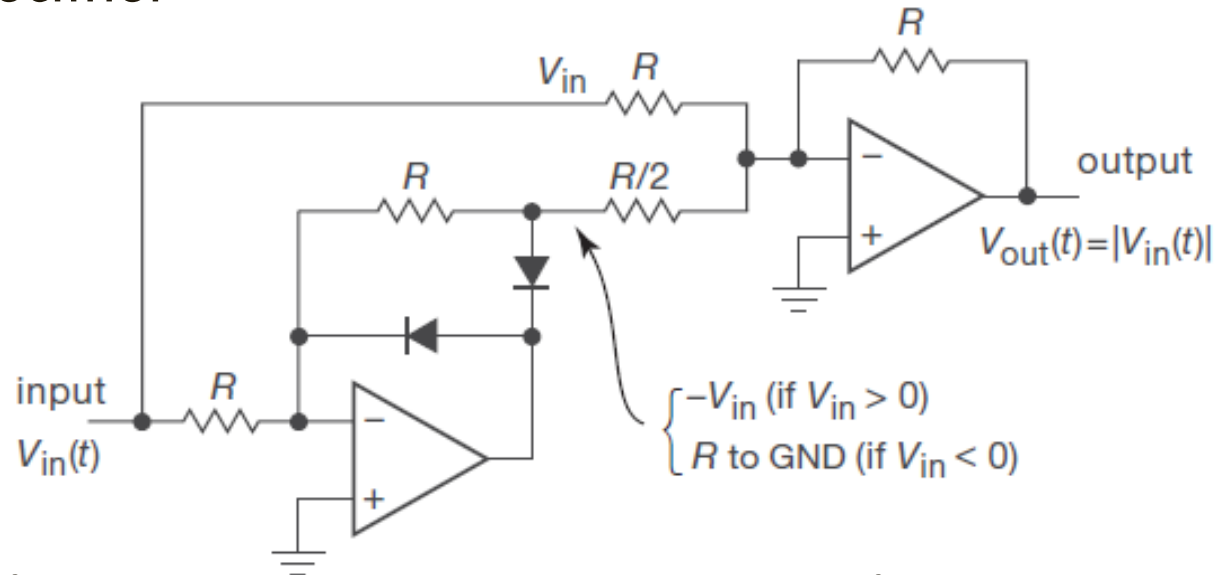




## □ Logarithmic Amplifier: add output stage with diode feedback

■ Ebers-Moll relation:  $I_D = I_o \exp\left(\frac{V_D}{nV_T}\right) - I_o$


■ Valid for  $V_D > 0$

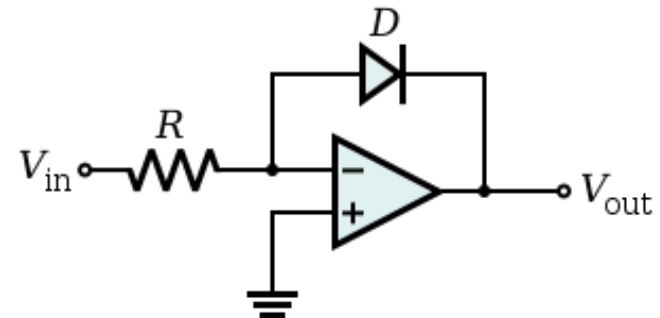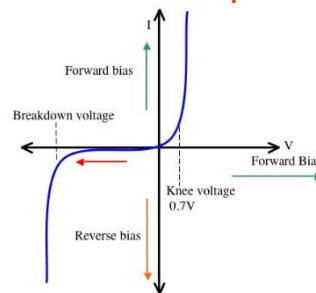


# Instrumentation Amplifier

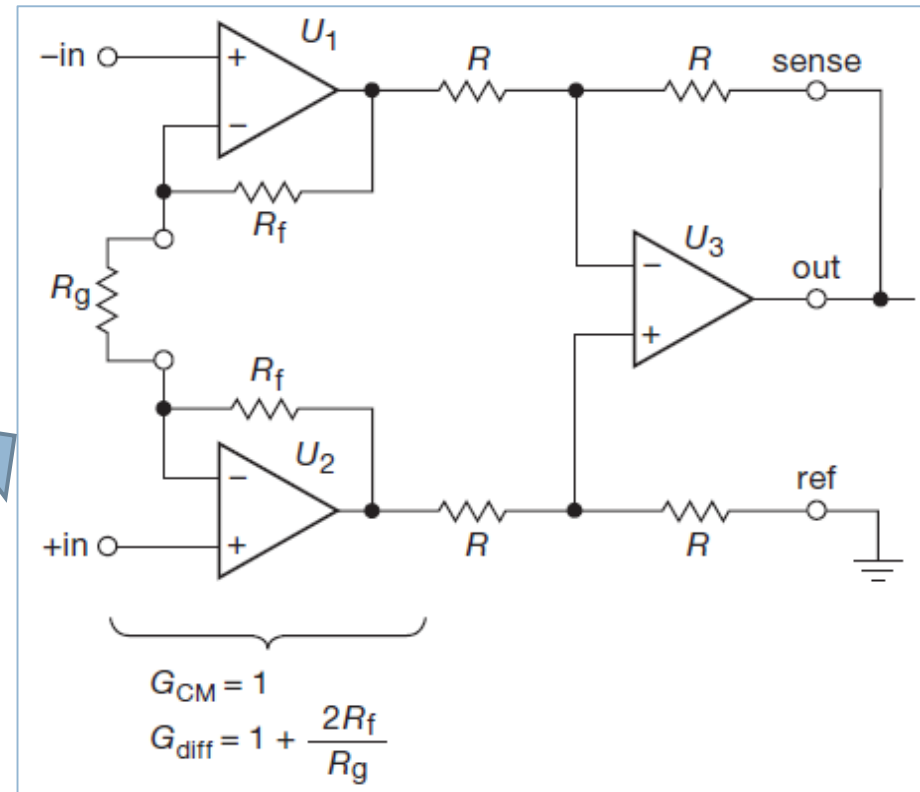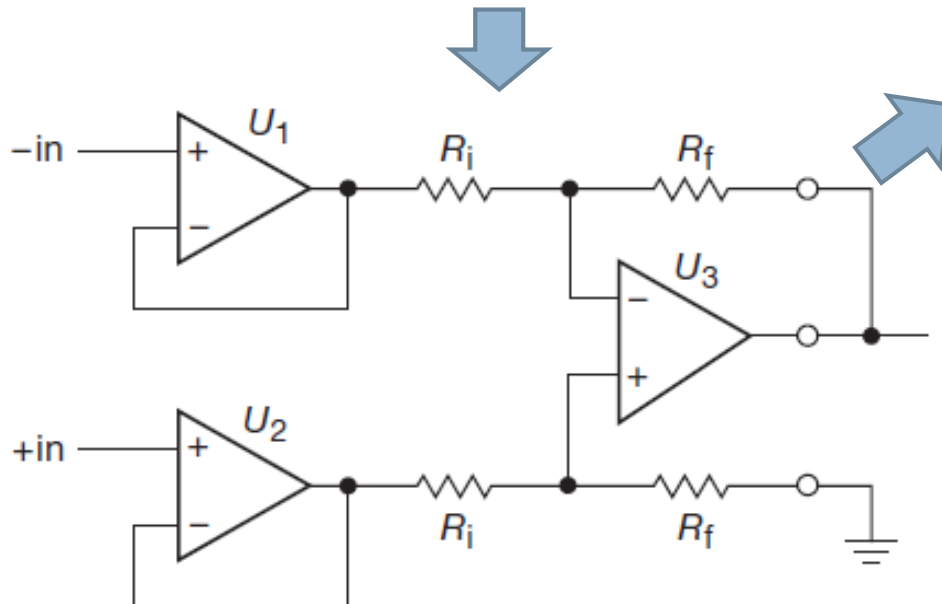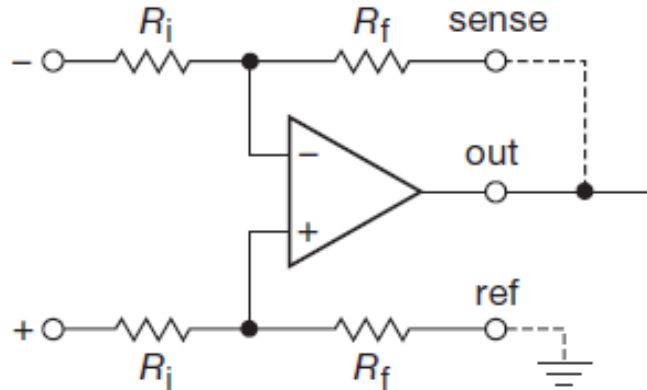

# Practical Example: AD620

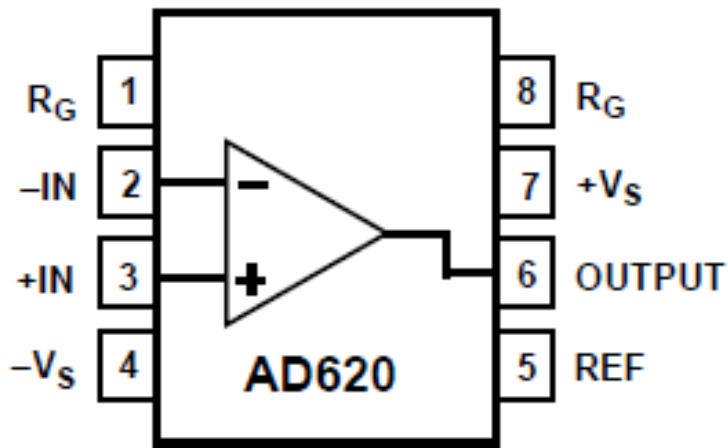

$$G = \frac{49.4k\Omega}{R_G} + 1$$

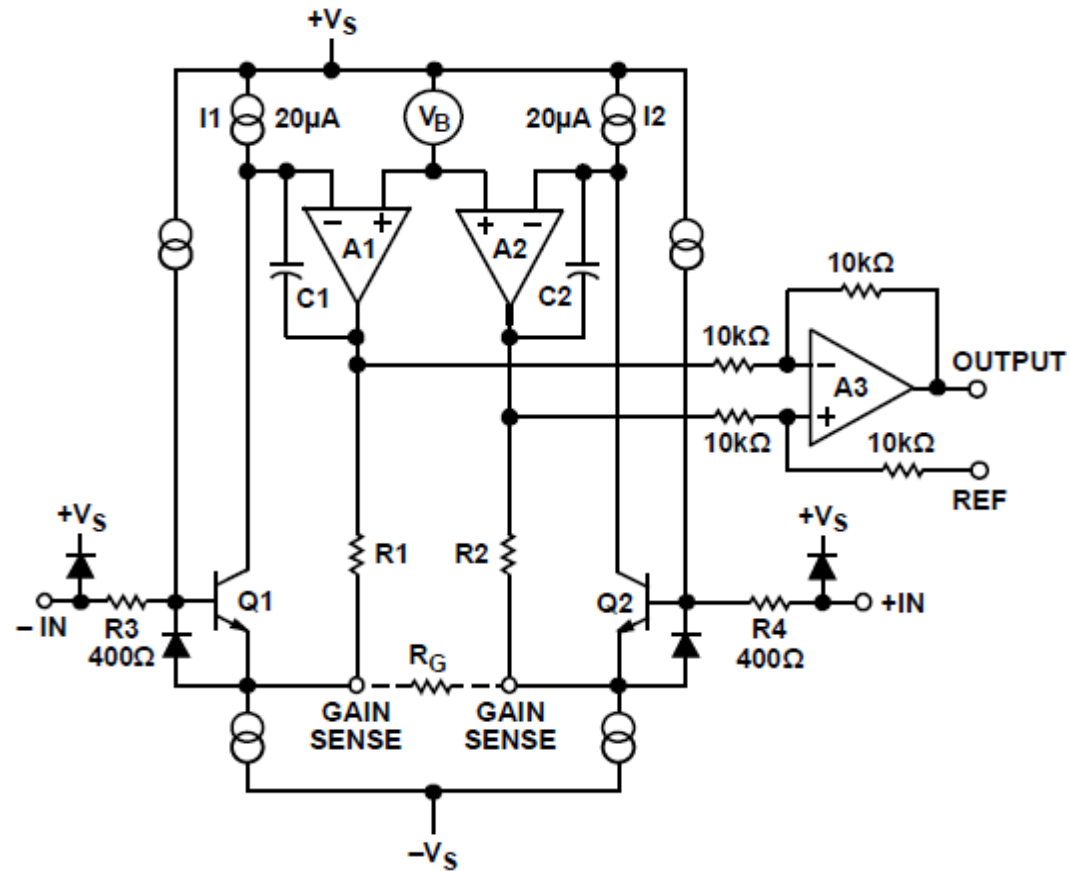

# Final Notes for Op Amp Circuits

- Check practical limitations to ensure validity of Op Amp rules
- Feedback must be arranged so that it is negative
  - ▣ *Must not mix up inverting and noninverting inputs*
- There must always be feedback at dc in op-amp circuit
  - ▣ *Otherwise op-amp is guaranteed to go into saturation*

# Reading Assignment

---

- Read Chapters 4, 5.15 of *Art of Electronics*