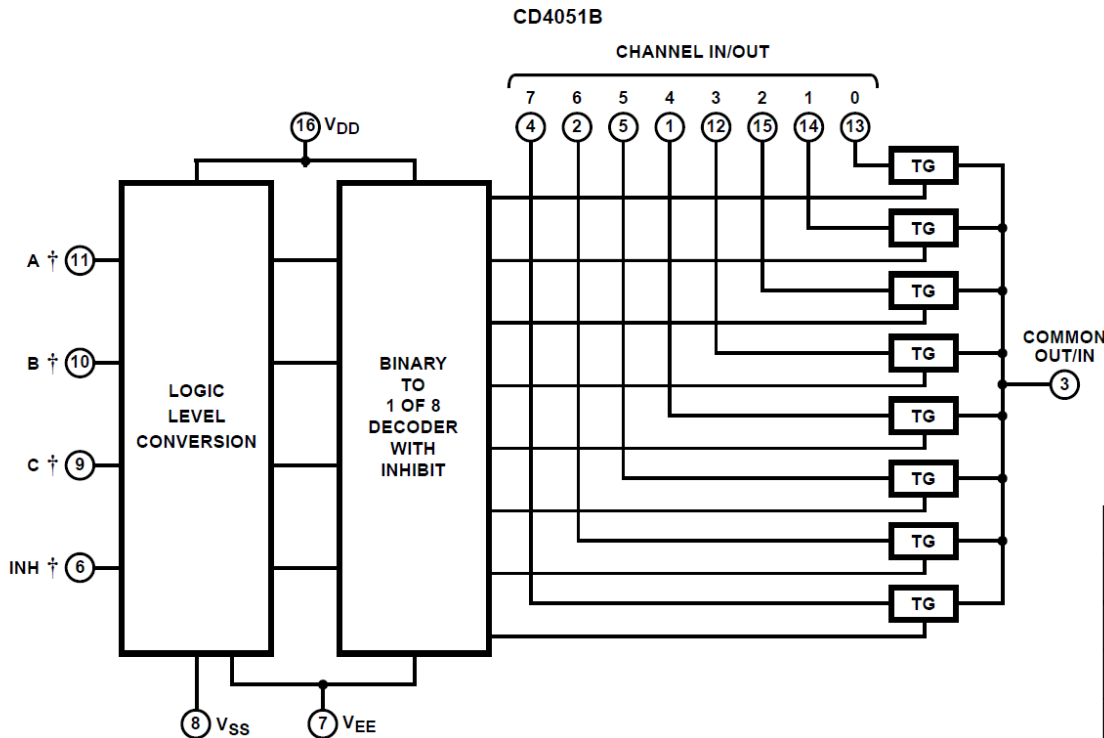


# ELECTRONIC SYSTEM DESIGN

## PART 2: BASIC ELECTRONIC INTEGRATED CIRCUITS AND THEIR APPLICATIONS

Prof. Yasser Mostafa Kadah

# Analog Multiplexer/Demultiplexer



- Wide Range of Digital and Analog Signal Levels
  - Digital ..... 3V to 20V
  - Analog .....  $\leq 20V_{P-P}$
- Low ON Resistance, 125 $\Omega$  (Typ) Over 15V<sub>P-P</sub> Signal Input Range for  $V_{DD}-V_{EE} = 18V$
- High OFF Resistance, Channel Leakage of  $\pm 100pA$  (Typ) at  $V_{DD}-V_{EE} = 18V$


INPUT STATES				"ON" CHANNEL(S)
INHIBIT	C	B	A	
<b>CD4051B</b>				
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	X	X	X	None

# The 555 Timer


3
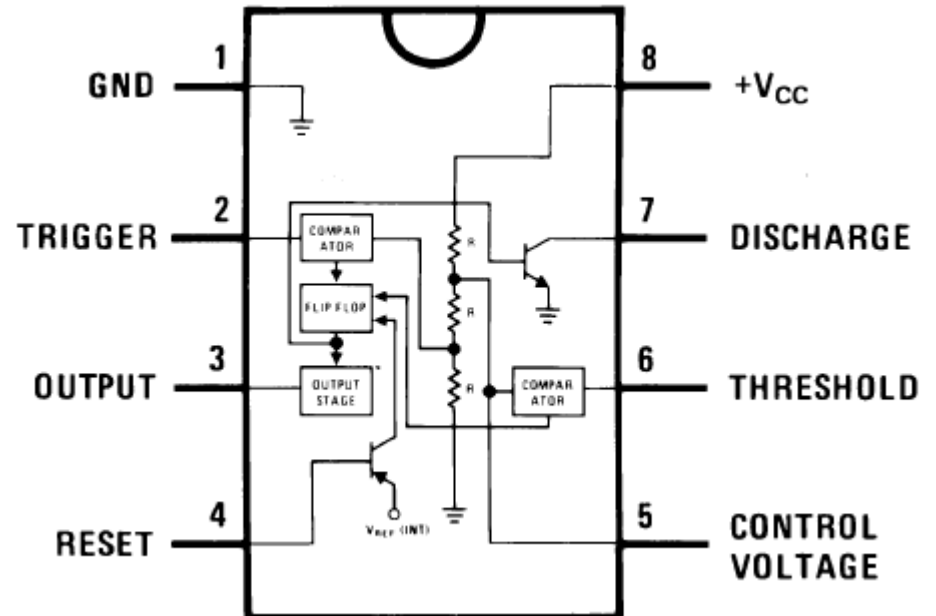
## Applications

- Precision timing
- Pulse generation
- Sequential timing
- Time delay generation
- Pulse width modulation
- Pulse position modulation
- Linear ramp generator




# 555: Monostable Operation

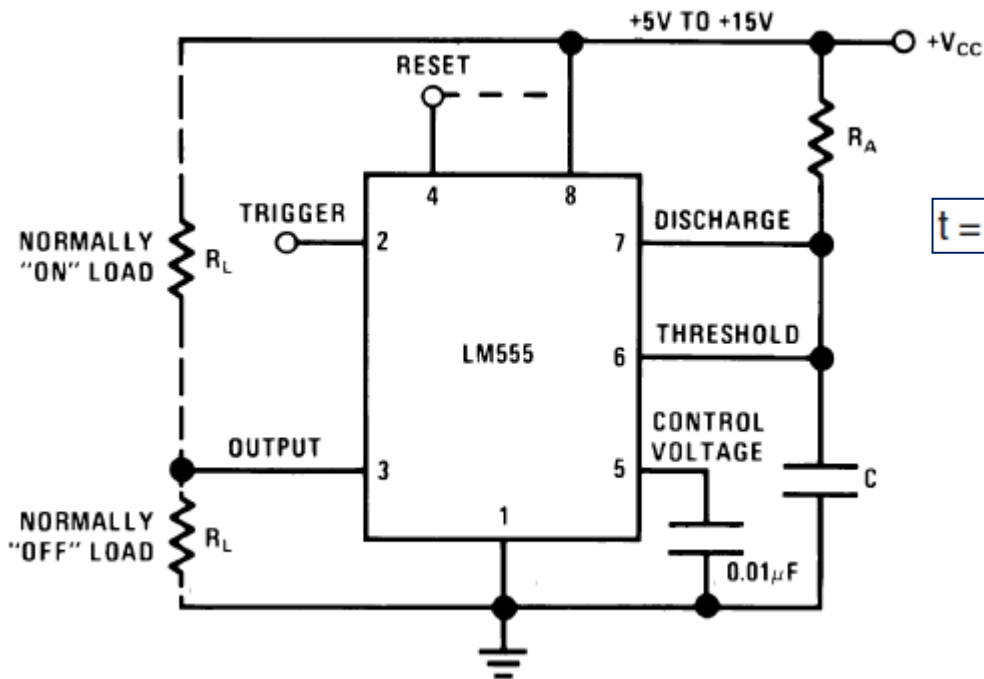



$$t = 1.1 R_A C$$

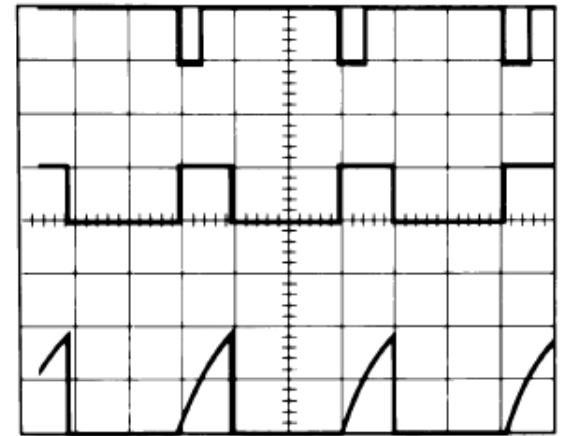$V_{CC} = 5V$   
 $TIME = 0.1 \text{ ms/DIV.}$   
 $R_A = 9.1k\Omega$   
 $C = 0.01\mu F$




00785106

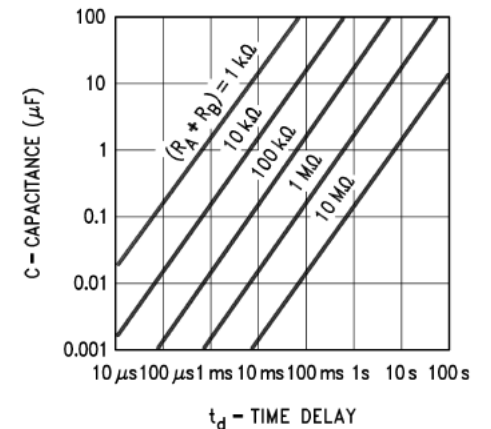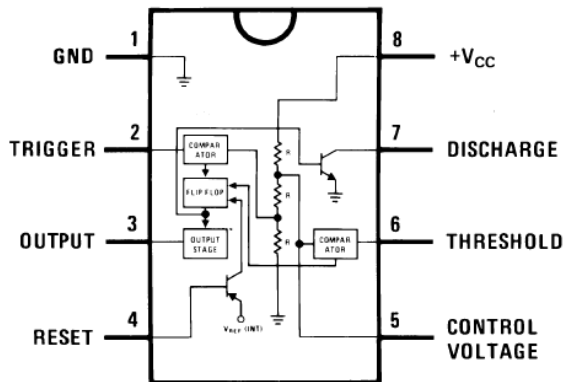Top Trace: Input 5V/Div.  
 Middle Trace: Output 5V/Div.  
 Bottom Trace: Capacitor Voltage 2V/Div.




# 555: Astable Operation

5

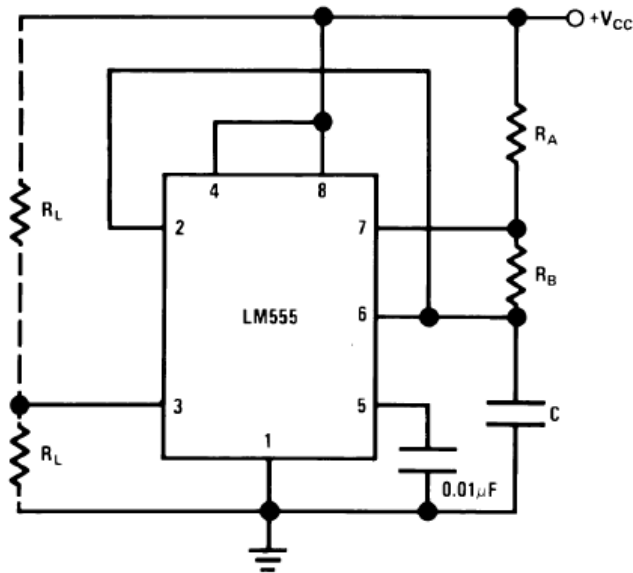

The duty cycle is:

$$D = \frac{R_B}{R_A + 2R_B}$$

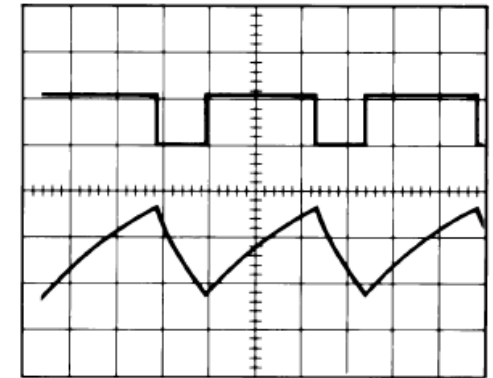

00785109

$V_{CC} = 5V$

TIME = 20µs/DIV.

$R_A = 3.9k\Omega$

$R_B = 3k\Omega$

$C = 0.01\mu F$

Top Trace: Output 5V/Div.

Bottom Trace: Capacitor Voltage 1V/Div.

The charge time (output high) is given by:

$$t_1 = 0.693 (R_A + R_B) C$$

And the discharge time (output low) by:


$$t_2 = 0.693 (R_B) C$$

Thus the total period is:

$$T = t_1 + t_2 = 0.693 (R_A + 2R_B) C$$

The frequency of oscillation is:

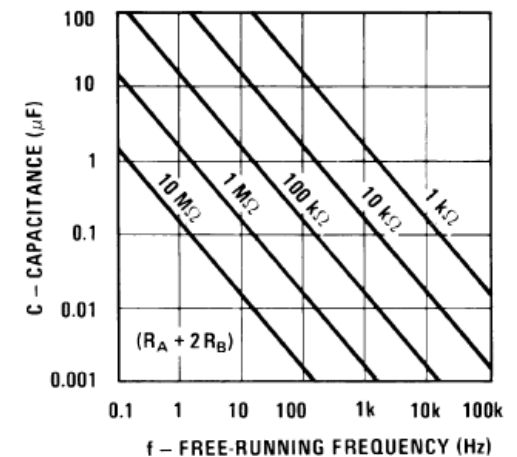
$$f = \frac{1}{T} = \frac{1.44}{(R_A + 2R_B) C}$$


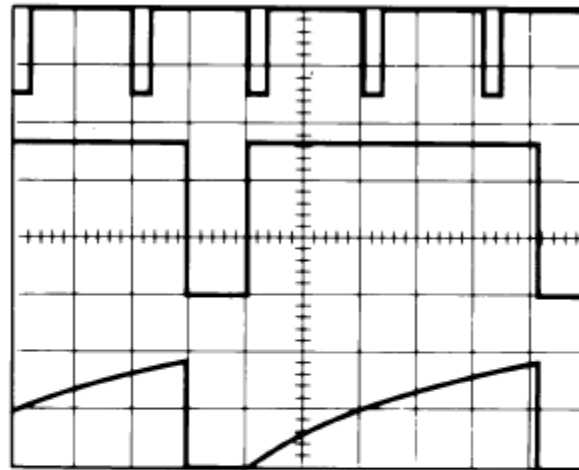
# 555: Frequency Divider

6

- Same as monostable operation circuit
  - ▣ Adjustment of period to be long enough



00785111

$V_{CC} = 5V$

TIME = 20 $\mu$ s/DIV.

$R_A = 9.1k\Omega$

$C = 0.01\mu F$



Top Trace: Input 4V/Div.

Middle Trace: Output 2V/Div.

Bottom Trace: Capacitor 2V/Div.

# 555: Pulse Width Modulator

7

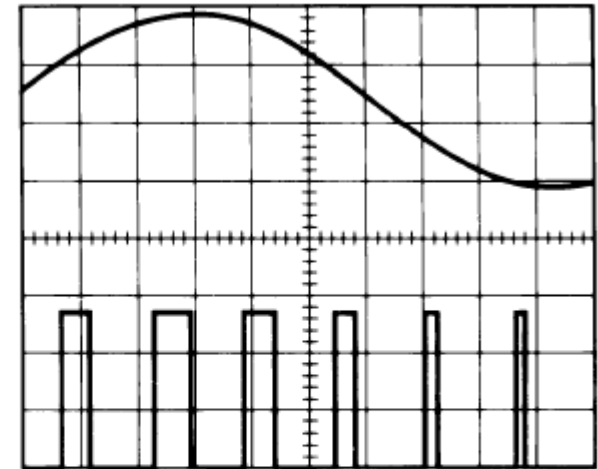
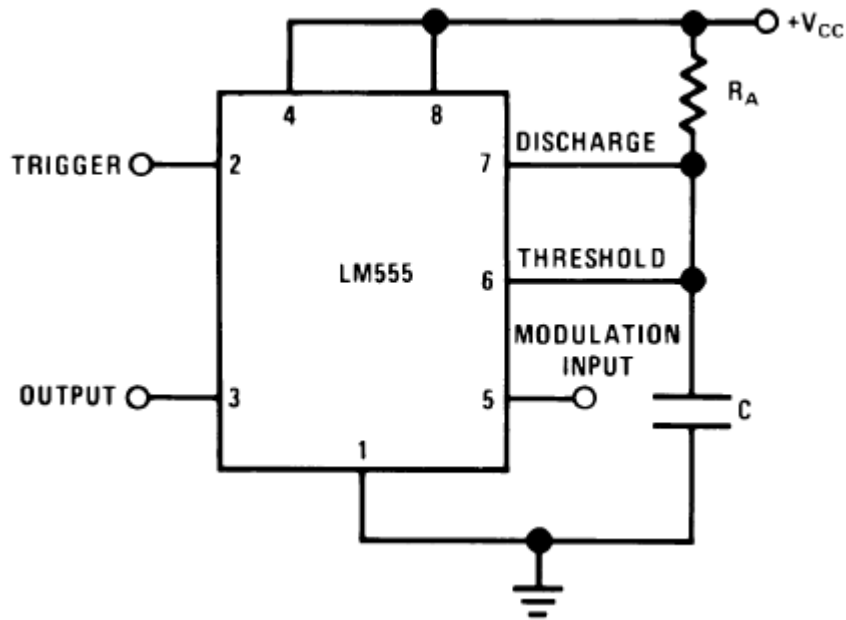


00785113

$V_{CC} = 5V$   
TIME = 0.2 ms/DIV. Top Trace: Modulation 1V/Div.  
Bottom Trace: Output Voltage 2V/Div.  
 $R_A = 9.1k\Omega$   
 $C = 0.01\mu F$



# Optocoupler/Optoisolator/Optotriac

- Digital
- Transistor
- Triac/SCR

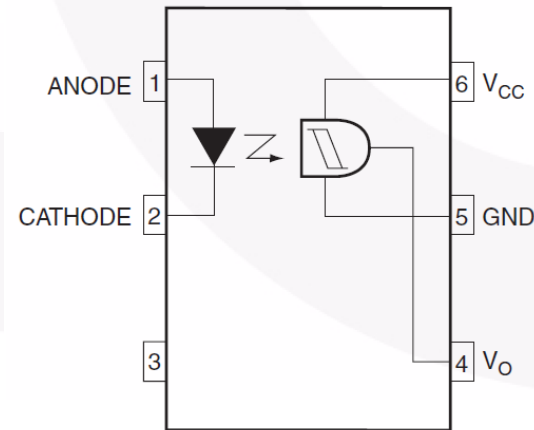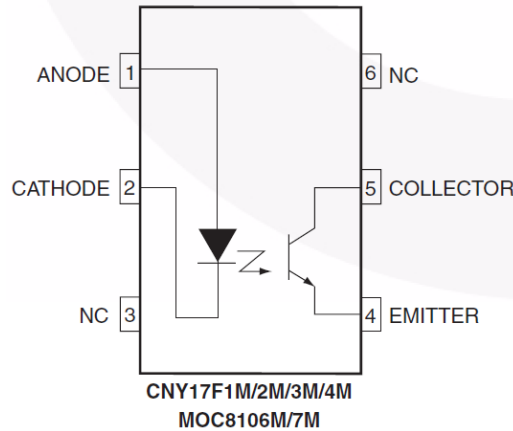

Truth Table

Input	Output
H	L
L	H

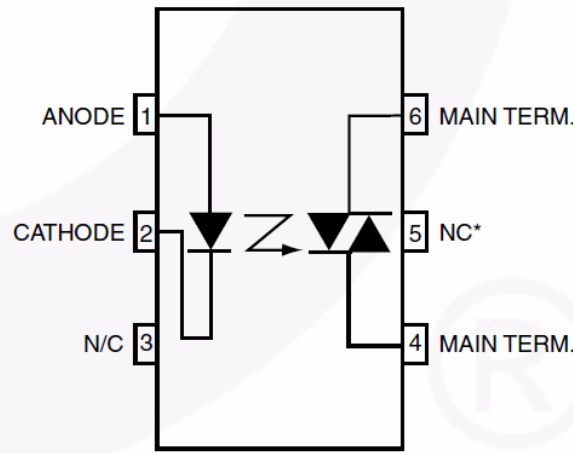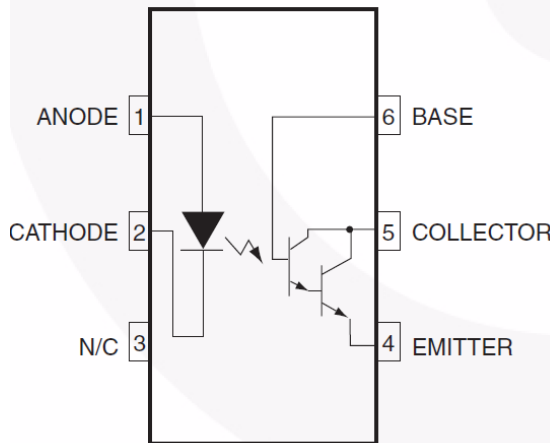

\*DO NOT CONNECT  
(TRIAC SUBSTRATE)





# Assignments

9

- Buy and assemble a 4051 analog multiplexer circuit and test it in the lab.
- Buy a 555 timer chip and assemble and test the monostable, astable and pulse width modulation circuits.
- Buy an optoisolator and test its operation in the lab.
- Write a report on your experiments and submit to the TA.